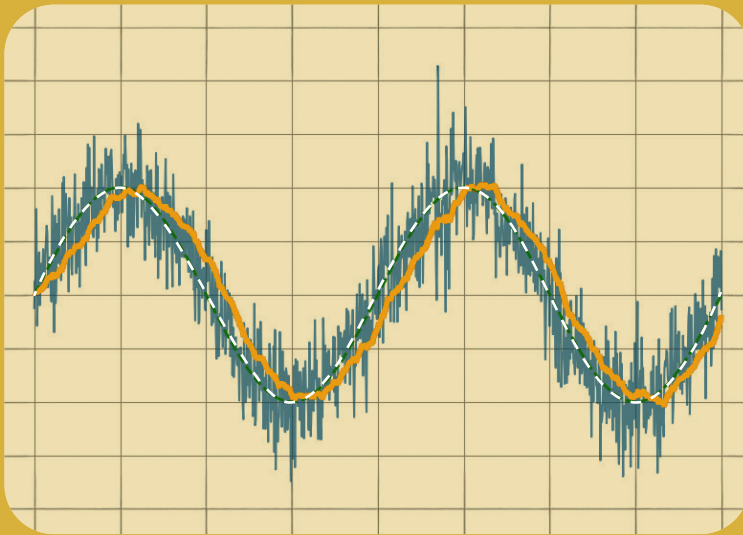


Introduction to Electronic Filters

Learn RC and RL Filters with Hands-On Circuits and Simulation



Academy Pro Title by
Peter Dalmaris, PhD

Introduction to Electronic Filters

Learn RC and RL Filters with
Hands-On Circuits and Simulation



Dr Peter Dalmaris

● This is an Elektor Publication. Elektor is the media brand of Elektor International Media B.V.
PO Box 11, NL-6114-ZG Susteren, The Netherlands
Phone: +31 46 4389444

● All rights reserved. No part of this book may be reproduced in any material form, including photocopying, or storing in any medium by electronic means and whether or not transiently or incidentally to some other use of this publication, without the written permission of the copyright holder except in accordance with the provisions of the Copyright Designs and Patents Act 1988 or under the terms of a licence issued by the Copyright Licensing Agency Ltd., 90 Tottenham Court Road, London, England W1P 9HE. Applications for the copyright holder's permission to reproduce any part of the publication should be addressed to the publishers.

● **Declaration**

The material in this publication is of the nature of general comment only, and does not represent professional advice. It is not intended to provide specific guidance for particular circumstances and it should not be relied on as the basis for any decision to take action or not take action on any matter which it covers. Readers should obtain professional advice where appropriate, before making any such decision. To the maximum extent permitted by law, the author and publisher disclaim all responsibility and liability to any person, arising directly or indirectly from any person taking or not taking action based on the information in this publication.

● **ISBN 978-3-89576-698-5** Print
ISBN 978-3-89576-699-2 eBook

● © Copyright 2025 Elektor International Media
www.elektor.com
Editor: Clemens Valens
Prepress Production: D-Vision, Julian van den Berg
Printers: Ipskamp, Enschede, The Netherlands

Elektor is the world's leading source of essential technical information and electronics products for pro engineers, electronics designers, and the companies seeking to engage them. Each day, our international team develops and delivers high-quality content - via a variety of media channels (including magazines, video, digital media, and social media) in several languages - relating to electronics design and DIY electronics. www.elektormagazine.com

Contents

Preface	7
Chapter 1 • Introduction	9
1.1 Course Overview and Objectives	9
1.2 Review of software and hardware	10
Chapter 2 • What is a filter?	13
2.1 Introduction to filters	13
2.2 First-order filters in real life applications	17
2.3 The four filters: low-pass, high-pass, band-pass, band-stop	19
2.4 Example: Compare a filtered and unfiltered signal	23
Chapter 3 • Dive into first order RC and RL filters	27
3.1 Introduction	27
3.2 What is a first-order filter?	29
3.3 RC low-pass filter behaviour	31
3.4 RC high-pass filter behaviour	35
3.5 RL low-pass filter behaviour	38
3.6 RL high-pass behaviour	42
3.7 Voltage division in AC using reactance	45
3.8 Cutoff frequency	53
3.9 Phase shift	57
3.10 Phase Shift in the Time Domain	59
3.11 Effect of Capacitor Value on Phase Shift	61
3.12 Step response of first-order filters	64
3.13 Impulse response of first-order filters	67
3.14 Just in case... definitions	70
3.15 Activity 1: Calculate filter response at low, cutoff and high frequencies	75
3.16 Activity 2: Simulate sinusoidal input response in the time domain	81
3.17 Activity 3: Parameter variation study	90
3.18 Activity 4: Filter on a breadboard	94
Chapter 4 • Filter analysis with Bode plots and phasors	100
4.1 Introduction to filter analysis with Bode plots and Phasors	100
4.2 What is a Bode plot?	105
4.3 Example Bode plots	113
4.4 What are phasors?	123
4.5 Example phasor plots	128
4.6 Activity 1: Calculate Missing Component to Achieve Desired Phasor behaviour	137
4.7 Activity 2: Design an RL high-pass filter for a target cutoff frequency and sketch the Bode and phasor plots	144
4.8 Summary	157
Chapter 5 • Filter applications	158
5.1 Introduction	158
5.2 Time constant and its meaning	159

- 5.3 Activity 1: Time constant experiment 162
- 5.4 Impact of time constant on signal shape 167
- 5.5 Activity 2: Impact of the Time Constant on Signal Shape 173
- 5.6 Audio tone shaping 175
- 5.7 Activity 3: Hear the effect of filtering 181
- 5.8 Sensor signal conditioning 187
- 5.9 Activity 4: A noisy light sensor with a filter 190
- 5.10 Noise filtering 194
- 5.11 Activity 5: Remove mains humming noise. 196
- 5.12 Debouncing switches 201
- 5.13 Activity 6: Button debouncing on the breadboard 203
- 5.14 Analog smoothing of digital PWM signals 207
- 5.15 Activity 7: Smoothing of a PWM signal 209
- 5.16 Power supply filtering. 212
- 5.17 Activity 8: Design a filter for a microphone 216
- 5.18 Activity 9: Design a filter for a thermistor or photoresistor 219

- Chapter 6 • Cascading Filters and Filter Types 224**
 - 6.1 Why cascade filters? 224
 - 6.2 Cascading RC filters and second-order behaviour 224
 - 6.3 Activity 1: Cascading RC filters on the breadboard 229
 - 6.4 Band-pass filter. 231
 - 6.5 Activity 2: Band-pass filter on the breadboard 235
 - 6.6 Filter design constraints: loading, attenuation, bandwidth 236
 - 6.7 Activity 3: Design a two-stage filter to isolate a frequency band 240
 - 6.8 Activity 4: Simulate cascaded filters with varying cutoff frequencies 244

- Chapter 7 • A primer on Python for filter analysis. 250**
 - 7.1 Why use Python to learn electronics? 250
 - 7.2 Set up the Python environment. 251
 - 7.3 Python fundamentals for electronics simulations 254
 - 7.4 Essential NumPy for electronics. 258
 - 7.5 Visualisation with Matplotlib 262
 - 7.6 Understanding and modifying electronics simulation scripts 272
 - 7.7 Additional resources. 276

- Chapter 8 • A primer of algebra for first-order filter analysis 278**
 - 8.1 Algebra in filter analysis 278
 - 8.2 Rearranging equations 279
 - 8.3 Ratios and proportions 282
 - 8.4 Manipulating fractions 284
 - 8.5 Powers and roots. 287
 - 8.6 Complex numbers 290
 - 8.7 Frequency, angular frequency, and substitution. 294
 - 8.8 Quick guide to simplifying transfer functions. 296
 - 8.9 Formula map. 300

- Index 302**

Preface

The idea for this book emerged from a simple observation: students often understand basic electronic components well but struggle when asked to apply that knowledge to real-world signal control problems. Filters, though conceptually straightforward, frequently appear abstract or unnecessarily complicated when introduced solely through mathematical formalisms. Yet, filters are everywhere, quietly performing critical functions in audio equipment, communication devices, industrial sensors, and embedded systems. I wrote this book to address this gap. My goal is to teach first-order filters in a way that is both rigorous and approachable, blending theory with hands-on practice. Rather than treating first-order filters as a brief stepping stone towards more complex subjects, this book treats them as powerful tools that deserve careful attention in their own right. Throughout this book, you will find a continuous emphasis on practice. You will use Python scripts to simulate circuits, online simulators to quickly prototype designs, and real-world breadboard experiments to observe circuit behaviour with oscilloscopes and spectrum analysers. This combination of simulation and physical experimentation is intended to make the material tangible and memorable. It is through building, observing, and analysing that theory becomes truly internalised.

This book assumes that you are already familiar with the fundamentals of electronics, particularly the behaviour of resistors, capacitors, and inductors, as well as basic circuit analysis techniques. If you have completed the Introduction to Electronics course or possess similar knowledge, you are fully prepared to embark on the journey ahead. Learning about filters is not only about gaining technical skills. It is also about learning to think critically about signals, noise, and system behaviour. It is about recognising the subtle but vital roles that small circuits play in the reliability and performance of much larger systems. My hope is that, by the end of this book, you will not only know how to design and analyse first-order filters, but also appreciate their elegance and importance in the broader context of electronics. I encourage you to approach the material with curiosity and patience. Build the circuits, run the simulations, question the results, and take the time to explore the behaviour of filters beyond the examples provided. The deeper your engagement with the material, the stronger and more intuitive your understanding will become. Welcome to the study of first-order filters. I am excited to be your guide on this practical and rewarding journey.

This book is designed to be both a study guide and a practical reference. To gain the maximum benefit from the material, it is important to approach it as an active participant rather than a passive reader. Each chapter builds systematically on the knowledge and skills introduced earlier. Concepts are introduced progressively, beginning with a general understanding of filters and their classifications, and moving towards detailed analyses and practical experiments with first-order filter circuits. It is recommended that you read the chapters sequentially, as each topic prepares the foundation for the next. Wherever simulations are presented, you are encouraged to run the provided Python scripts on your own system. These simulations allow you to visualise filter behaviours that are difficult to grasp from static text alone. The scripts are designed to be clear and accessible, even for readers with only basic Python programming experience. Modifying the parameters and

observing how the results change is an excellent way to deepen your understanding. You will find all Python scripts on Github at https://github.com/futureshocked/introduction_to_electronics_filters

In addition to Python simulations, many examples reference online circuit simulators. These simulators allow you to experiment with filter circuits interactively. It is highly recommended that you reproduce these circuits yourself, adjust component values, and observe how these changes affect circuit behaviour. This hands-on exploration will reinforce the theoretical principles discussed in the text.

Real-world experiments form another vital component of the learning experience. When possible, you should construct the simple filter circuits described in the book on a breadboard. Using basic laboratory instruments such as oscilloscopes and spectrum analysers, you will be able to observe signal behaviour directly. These experiments are chosen to be accessible with modest equipment, yet they provide invaluable experience in measurement and analysis. As you work through the material, it is important to keep a notebook or digital journal of your observations, measurements, and conclusions. Reflecting on what you observe, especially when simulation results differ from physical measurements, will build a deeper and more critical understanding of electronic behaviour.

Finally, although this book focuses specifically on first-order filters, you will occasionally encounter references to second-order filters and more advanced topics. These references are included to provide context and to prepare you for future learning. However, it is not necessary to understand higher-order filters in detail before mastering the first-order designs presented here. Your success with this book depends less on speed and more on deliberate practice. Take the time to build, test, and truly understand each circuit. By doing so, you will develop both the theoretical knowledge and the practical confidence that define an effective electronics practitioner.

If you have found an error, please let me know. Go to <https://connect.techexplorations.com/bugs/introduction-to-electronics>, and fill in the form. I'll get it fixed and update the book.