

Build Your Own Software-Defined Radio

Practical Guide to Modular RF Design



Thomas Duden

Build Your Own Software-Defined Radio

Practical Guide to Modular RF Design



Thomas Duden

● This is an Elektor Publication. Elektor is the media brand of Elektor International Media B.V.
PO Box 11, NL-6114-ZG Susteren, The Netherlands
Phone: +31 46 4389444

● All rights reserved. No part of this book may be reproduced in any material form, including photocopying, or storing in any medium by electronic means and whether or not transiently or incidentally to some other use of this publication, without the written permission of the copyright holder except in accordance with the provisions of the Copyright Designs and Patents Act 1988 or under the terms of a licence issued by the Copyright Licensing Agency Ltd., 90 Tottenham Court Road, London, England W1P 9HE. Applications for the copyright holder's permission to reproduce any part of the publication should be addressed to the publishers.

● Declaration

The author, editor, and publisher have used their best efforts in ensuring the correctness of the information contained in this book. They do not assume, and hereby disclaim, any liability to any party for any loss or damage caused by errors or omissions in this book, whether such errors or omissions result from negligence, accident or any other cause. All the programs given in the book are Copyright of the Author and Elektor International Media. These programs may only be used for educational purposes. Written permission from the Author or Elektor must be obtained before any of these programs can be used for commercial purposes.

● **ISBN 978-3-89576-710-4** eBook

● © Copyright 2026 Elektor International Media
www.elektor.com
Editor: Glauceleine Vieira

Elektor is the world's leading source of essential technical information and electronics products for pro engineers, electronics designers, and the companies seeking to engage them. Each day, our international team develops and delivers high-quality content - via a variety of media channels (including magazines, video, digital media, and social media) in several languages - relating to electronics design and DIY electronics. www.elektormagazine.com

Contents

Chapter 1 • Introduction	9
Chapter 2 • Mechanics	11
2.1 The RF Brick Template	11
2.2 The Chassis	16
2.3 The 19 Inch Module Carrier	18
2.4 Concluding Remarks	21
Chapter 3 • Bridges	23
3.1 The USB Isolator Bridge	23
3.2 I2C Level Shifter Bridge	27
3.3 The I ² C Power Switch Bridge	29
3.4 Examples of the Use of Bridges	32
Chapter 4 • Signal Chains with RF Bricks	34
4.1 The Antenna	34
4.1.1 What the antenna does not receive, no amplifier can pick up from the noise . . .	35
4.1.2 An antenna belongs outside	35
4.1.3 Lightning and surge protection is essential	35
4.1.4 An Antenna has frequency-dependent properties	35
4.1.5 The Symmetrical feed line avoids common mode interference	36
4.1.6 Signal cosmetics	37
4.2 The Band Filter Brick	37
4.2.1 Excursus: working with the NanoVNA	39
4.2.1.1 Installing the NanoVNA software on the host	41
4.2.1.2 Calibration of the NanoVNA	43
4.2.2 Calculating filter data yourself	45
4.2.3 Structure of an example filter	53
4.2.3.1 Winding the toroidal coil according to the table	54
4.2.3.2 Measuring the inductance, adjusting the number of turns	54
4.2.3.3 Set up the first resonant circuit, measure resonant frequency	54
4.2.3.4 Set up the second resonance circuit and measure the resonance point	56
4.2.3.5 Set up and adjustment of the resonant parallel circuit (not tapped)	57

- 4.2.3.6 Set up and adjust the tapped parallel circuit 60
- 4.2.3.7 Compensating for the pole 61
- 4.3 The Preamplifier Brick 64
- 4.4 The PLL Brick 67
- 4.5 The Lima Demodulator Brick 71
- 4.6 The Integrated Double Demodulator 74
- 4.7 The Direct Conversion Signal Chain 76
- 4.8 The Multiband Direct Conversion RX. 79
- 4.9 The 45MHz Narrow Band Brick 84
 - 4.9.1 The double superhet signal chain 85
- Chapter 5 • Bricks for RF Measurements 87**
 - 5.1 Test Signals – One Single Spectral Line 87
 - 5.2 Test Signals - Two Spectral Lines 88
 - 5.2.1 The Low Distortion Generator Brick. 89
 - 5.2.2 The Wheatstone-bridge power combiner 91
 - 5.3 Test Signals — Noise 95
 - 5.3.1 5 Hz Bandwidth cut from the center, please 95
 - 5.3.2 The noise power ratio (NPR). 97
 - 5.3.3 The notch filter brick. 97
 - 5.3.4 Alternatives to NPR measurement with the notch filter 107
 - 5.3.5 What information do the different approaches provide? 108
 - 5.3.6 The noise generator brick 108
 - 5.3.7 The broadband amplifier brick with MMICs. 115
 - 5.3.8 The noise bridge. 118
- Chapter 6 • Useful Accessories 121**
 - 6.1 The ATU-100 Antenna Tuner 121
 - 6.1.1 Changing the firmware of the ATU-100 123
 - 6.1.2 The Mechanical Model 125
 - 6.2 The X-Phase QRM Eliminator. 126
 - 6.2.1 Compensating the QRM 126
 - 6.2.2 Reverse polarity protection and fuse protection 128

6.2.3 Assembly	129
6.2.4 Operating the X-Phase QRM Eliminator	130
Chapter 7 • Cables and Wires	131
Chapter 8 • Sound Cards	133
8.1 The Internal Sound Card	133
8.2 USB Stick with 24-Bit Sound Card (CM6533)	134
8.3 Asus Xonar U7 MKII	135
8.4 Behringer U-PHORIA UMC404HD	137
8.5 Conclusion	140
Chapter 9 • PC Host Software	141
9.1 SoapySDR	141
9.1.1 Tweaking the SoapyAudio module	143
9.1.2 Adapt SoapyAudio to the new rtaudio7	149
9.2 GQRX	157
9.2.1 Integrated tuning with gqr-hamlib	163
9.2.2 Compile GQRX yourself	167
9.2.3 Adding additional functionality to GQRX	173
9.2.4 tweak gqr-hamlib	176
9.2.5 Increase the bandwidth of PulseAudio	180
9.3 CubicSDR	183
9.4 SDRPP	191
9.5 Summary	194
Chapter 10 • GnuRadio	196
10.1 Control the SDR Hardware with GnuRadio	196
10.1.1 Create the Python Arduino control block	197
10.2 Installing the First GUI Elements	206
10.2.1 FrequencySink and Waterfall Sink	206
10.2.2 Controlling the frequency display with messages	211
10.2.3 Using the frequency selector	214
10.3 SSB Demodulation	215
10.3.1 The Weaver scheme	216

- 10.3.2 GUI Gain Controls 220
- 10.3.3 Improved Weaver scheme 221
- 10.3.4 Optimized messaging 223
- 10.3.5 Adjustable filter bandwidth. 225
- 10.4 Control More Hardware Options via the Arduino. 226
 - 10.4.1 Expanding the TS850-CAT interface in the Arduino 226
 - 10.4.2 Extending the serial control block 229
- 10.5 Once Again: Optimize the Messaging 231
- 10.6 Cleaning Up the GUI 233
- 10.7 Summary and Outlook 234
- Chapter 11 • “SDR” with FPGAs. 235**
 - 11.1 VHDL 235
 - 11.2 Select FPGA and IDE 236
 - 11.3 Select the Data Converter. 237
 - 11.4 Learn How to Use Scilab 238
 - 11.4.1 Install Scilab 238
 - 11.5 Installing the FPGA Toolchain 239
 - 11.5.1 Install the latest Intel® Quartus version 239
 - 11.5.2 Starting the help system 242
 - 11.5.3 Install the Arrow programmer 244
 - 11.6 Bringing the FPGA to life. 245
 - 11.6.1 Setting up the FPGA shield 245
 - 11.6.2 Hello World – make an LED flash. 248
 - 11.6.2.1 Configure the project 248
 - 11.6.2.2 Create a block diagram from standard functions 250
 - 11.6.2.3 Define the timing constraints. 264
 - 11.6.2.4 Synthesizing the design 265
 - 11.6.2.5 Using the pin planner 266
 - 11.6.2.6 Finalizing the synthesis. 268
 - 11.6.2.7 Loading the design into the FPGA temporarily 269
 - 11.6.2.8 Loading the design permanently into the FPGA 271

Chapter 12 • Developing Blocks for PC-Independent FPGA Receivers with SSB/CW Filters	273
12.1 The Delta Sigma DAC	273
12.1.1 Simplified principle of operation	273
12.1.2 Translation into VHDL	274
12.1.3 Define the DAC block.	275
12.2 A Simple Sine Wave Generator	278
12.2.1 Realization - CORDIC or value table ?	278
12.2.2 Translation into VHDL code	281
12.2.3 Create the sine generator block	282
12.2.4 Testing the sine wave generator block with the DAC	282
12.3 The Differential Amplifier Brick	283
12.4 The 24-bit ADC	285
12.4.1 Setting up the 24-bit ADC brick	285
12.4.2 Reading out the ADC with VHDL	287
12.5 A Signal Chain for SSB Demodulation.	290
12.5.1 Quadrature Sampling	291
12.5.2 The first FIR low-pass filter	293
12.5.3 The Weaver mixer	300
12.5.4 The second FIR low-pass filter	302
12.5.5 Assembling the signal chain	302
12.6 The GnuRadio Flowgraph	303
12.7 Optimizations	304
12.7.1 The Anti-Aliasing Filter.	305
12.7.2 Inserting a peak value detector	308
12.7.3 Matching the narrowband signal chain brick to the system impedance.	309
12.7.4 Quadruple oversampling with the LTC2380.	312
12.7.5 Tenfold oversampling with the LTC2380	315
12.7.6 Analyzing the effect of oversampling	318
12.7.7 Interpreting the Weaver signal chain as an oversampling filter	321
Chapter 13 • Outlook	322
Chapter 14 • Sources	323